

Комментарии к задаче 5.3

$$\textcircled{1} \quad \omega L_H \frac{di_H}{d\omega} + i_H R_H = \pm E_d \quad \left| \text{Задача 5.3} \right|$$

$$i_H = \pm \frac{E_d}{R_H} \left(1 - \frac{2e^{-\omega/\omega_T}}{1 + e^{-\omega/\omega_T}} \right) = \pm \frac{E_d}{R_H} \left(1 - \frac{2e^{-\omega t/\omega_T}}{1 + e^{-\omega t/\omega_T}} \right) =$$

$$= \pm \frac{E_d}{R_H} \left(1 - \frac{2e^{-t/\tau}}{1 + e^{-t/\tau}} \right) \quad \frac{\omega T}{2} = \frac{2\pi}{T} \cdot \frac{T}{2} = \pi$$

$$i = \frac{I}{2} \quad I_{\max} = \pm \frac{E_d}{R_H} \left(\frac{1 + e^{-T/2\tau} - 2e^{-T/2\tau}}{1 + e^{-T/2\tau}} \right)$$

$$I_{\max} = \frac{E_d}{R_H} \frac{(1 - e^{-T/2\tau})}{(1 + e^{-T/2\tau})} \quad \tau = \frac{L}{R} =$$

$$= 2,5 \cdot 10^{-3} \text{ c}$$

$$I_{\max} = \frac{10}{0,4} \frac{1 - e^{-2}}{1 + e^{-2}} = 16 \text{ A}$$

(к задаче 5.3) ①

$$\dot{I}_H - \frac{E_d}{R_H} = - \frac{2E_d}{R_H} \frac{e^{-t/\tau}}{1 + e^{-T/2\tau}}$$

дано: $\tau = T/2$
 найти: $\dot{I}_H$
 решение: $\dot{I}_H = \frac{E_d}{R_H} - \frac{2E_d}{R_H} \frac{e^{-t/\tau}}{1 + e^{-T/2\tau}}$

$$\dot{I}_H - \frac{E_d}{R_H} = \frac{E_d}{R_H} e^{-t/\tau} - \frac{E_d}{R_H} e^{-t/\tau} - \frac{2E_d}{R_H} \frac{e^{-t/\tau}}{1 + e^{-T/2\tau}}$$

$$\dot{I}_H - \frac{E_d}{R_H} = \left(-\frac{E_d}{R_H} + \frac{E_d}{R_H} - \frac{2E_d}{R_H} \frac{e^{-t/\tau}}{1 + e^{-T/2\tau}} \right) e^{-t/\tau}$$

$\left(-\frac{2E_d}{R_H} \frac{e^{-t/\tau}}{1 + e^{-T/2\tau}} \right) \leftarrow -I_{max}$

$$\dot{I}_H - \frac{E_d}{R_H} = \left(-I_{max} - \frac{E_d}{R_H} \right) e^{-t/\tau}$$

$$\dot{I}_H = \left(-I_{max} - \frac{E_d}{R_H} \right) e^{-t/\tau} + \frac{E_d}{R_H}$$

$$i(t) = \left(-I_{max} - \frac{E_d}{R}\right) e^{-t/\tau} + \frac{E_d}{R}$$

$$t_1 = ? \quad i(t) = 0$$

$$0 = \left(-I_{max} - \frac{E_d}{R}\right) e^{-t_1/\tau} + \frac{E_d}{R}$$

$$e^{-t_1/\tau} = \frac{-E_d/R}{I_{max} + \frac{E_d}{R}} = \frac{E_d/R}{\frac{E_d}{R} + I_{max}}$$

$$-t_1/\tau = \ln \frac{E_d/R}{\frac{E_d}{R} + I_{max}}$$

$$+ t_1 = -\tau \ln \frac{E_d/R}{\frac{E_d}{R} + I_{max}} \quad !$$